


Alex Baslins

Problem One: Consider the circuit shown for Problem One in the file above. (45 points)

The voltage source, V_A , and the current source, I_S , are each a constant dc source. The circuit has been operating for a long time with Switch One (S1) in the closed position prior to $t = 0$ and Switch Two (S2) in the open position prior to $t = 0$. Note; I do not provide numerical values for this problem. Thus, your answer should be expressed in terms of the given circuit elements. Please Note; in this problem, if you have an Req in your answer, please clearly define the Req term. (Thank-you).

1. Determine the expression for $i_L(t = 0')$. (5 points)
2. Determine the expression for $V_C(t = 0')$. (5 points)
3. Write the first order differential equation for $i_L(t)$ for $t > 0$, in standard form. (5 points)
4. Determine the complete solution for $i_L(t)$ for $t > 0$. (Please solve for all constant(s) and define τ) (10 points)
5. Write the first order differential equation for $V_C(t)$ for $t > 0$, in standard form. (5 points)
6. Determine the complete solution for $V_C(t)$ for $t > 0$. (Please solve for all constant(s) and define τ) (15 points)

PROBLEM ONE:

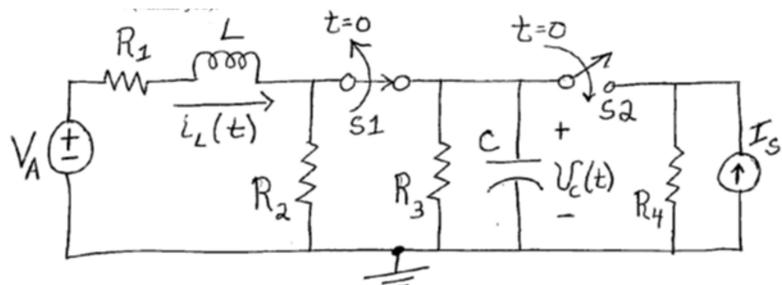

1.) $i_L(+ = 0')$



$$\text{Req} = \frac{R_2 R_3}{R_2 + R_3}$$

$$i_L(+ = 0') = \frac{V_A}{R_1 + \text{Req}}$$

2.) $V_C(+ = 0')$

V_C is charged so $V_C = V_A$

3.)

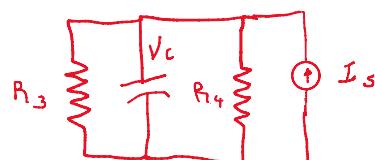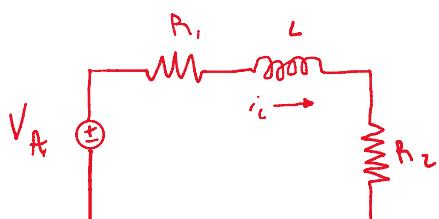



$$-V_A + R_1 i_L + L \frac{di_L}{dt} + R_2 i_L = 0$$

$$L \frac{di_L}{dt} + (R_1 + R_2) i_L = V_A$$

$$\frac{L}{(R_1 + R_2)} \frac{di_L}{dt} + i_L = \frac{V_A}{(R_1 + R_2)}$$

4.) $i_L = K e^{-\frac{t}{\tau}} + \frac{V_A}{(R_1 + R_2)}$


$\tau = \frac{L}{R_1 + R_2}$

$K = \frac{V_A}{(R_1 + R_{eq})}$

$R_{eq} = \frac{R_2 R_3}{R_2 + R_3}$

$$i_L = \left(\frac{V_A}{R_1 + R_{eq}} - \frac{V_A}{R_1 + R_2} \right) e^{-\frac{(R_1 + R_2)t}{L}} + \frac{V_A}{(R_1 + R_2)}$$

5.)

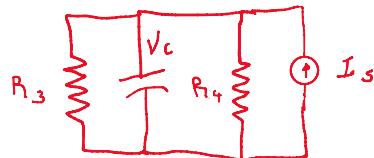

$$R_{eq} = \frac{R_3 R_4}{R_3 + R_4}$$

$$-I_S + \frac{V_C}{R_{eq}} + C \frac{dV_C}{dt} = 0$$

$$R_{eq} C \frac{dV_C}{dt} + V_C = I_S R_{eq}$$

6.)

6.)

$$V_c = K e^{-t/\tau} + I_s R_{eq} \quad t > 0$$

$$\tau = R_{eq} C$$

$$V_A = K + I_s R_{eq}$$

$$R_{eq} = \frac{R_3 R_4}{R_3 + R_4}$$

$$K = V_A - I_s R_{eq}$$

$$V_c = (V_A - I_s R_{eq}) e^{-\frac{t}{R_{eq}C}} + I_s R_{eq}$$

Problem Two: Consider the circuit shown for Problem Two in the file above. (30 points)

The circuit has been operating for a long time with the switch in the open position prior to $t = 0$. The voltage source, V_S , is a constant dc source.

- Write the second-order differential equation in standard form for the capacitor voltage $V_c(t)$ for $t > 0$. (Note; the only variable which should appear in your equation is $V_c(t)$). Please note; I do not provide numerical values for the resistor, capacitor, inductor, and the source. Thus, your answer should be expressed in terms of the given variables). (10 points)
- You are now given that this second-order circuit is **critically damped**. In addition, the following two initial conditions are given;

$$v_C(t = 0^+) = 0 \text{ Volts}$$

$$i(t = 0^+) = 0 \text{ Amps}$$

Determine the complete solution to this second-order circuit. As part of your solution, determine the two constants; K_1 and K_2 . (You do not have to solve for the value of "s"). (15 points total)


- For this part of the problem, you are now given the following values;

$$L = 100 \text{ mH}$$

$$C = 0.01 \mu\text{F}$$

Determine the value of the resistor R for the second-order system to be critically damped. (5 points)

PROBLEM TWO:

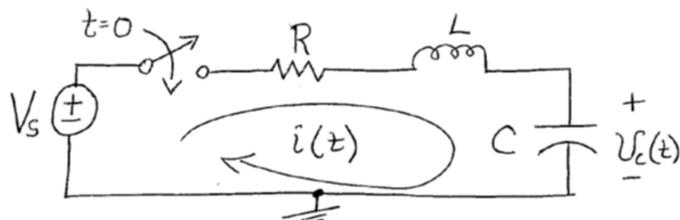

1.)

$$-V_S + R i(+) + L \frac{di(+)}{dt} + V_c(+) = 0$$

∴

$$-V_s + R i(t) + L \frac{di(t)}{dt} + V_c(t) = 0$$

$$i = C \frac{dV_c}{dt}$$

$$i' = C \frac{d^2 V_c}{dt^2}$$

$$LC \frac{d^2 V_c}{dt^2} + RC \frac{dV_c}{dt} + V_c = V_s$$

$$\frac{d^2 V_c}{dt^2} + \frac{R}{L} \frac{dV_c}{dt} + \frac{1}{LC} V_c = \frac{V_s}{LC}$$

2.)

Critically damped

$$\zeta = 1$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{\alpha}{\omega_0}$$

$$\zeta = \frac{R\sqrt{LC}}{2L} = \frac{R\sqrt{C}}{2\sqrt{L}}$$

$$\frac{R\sqrt{C}}{2\sqrt{L}} = 1$$

$$L = \frac{R^2 C}{4}$$

$$V_{c_n} = h_1 e^{st} + h_2 t e^{st}$$

$$V_{c_p} = V_s$$

$$V_c = k_1 e^{st} + k_2 t e^{st} + V_s$$

$$0 = k_1 + V_s$$

$$k_1 = -V_s$$

$$\frac{dV_c}{dt} = k_1 s e^{st} + k_2 + s t e^{st} + k_2 e^{st}$$

$$0 = k_1 s + k_2$$

$$k_2 = V_s s$$

$$V_c = -V_s e^{st} + V_s s t e^{st} + V_s$$

3.)

$$L = \frac{R^2 C}{4}$$

$$R^2 C = 4L$$

$$R = \sqrt{\frac{4L}{C}}$$

$$L = 100 \text{ mH.}$$

$$C = .01 \mu\text{F.}$$

$$R = \sqrt{\frac{4(100 \times 10^{-3})}{(.01 \times 10^{-6})}}$$

$$R = 6.3245 \text{ k}\Omega$$