

CPE 487 Midterm Exam (100 Points)


Due: October 18, 12:30pm

Signed *Alex Gaskins*

Date *10/17/2022*

**Part1:** By hands only

 - Complete the timing diagram of the following circuit by adding the timing trace for **f** and **g**:




8 Intervals

	a	b	c	AND	NAND	OR	NOR
1	0	0	0	0	1	0	1
2	1	0	0	0	1	1	0
3	0	1	0	0	1	1	0
4	1	1	0	0	1	1	0
5	0	0	1	0	1	1	0
6	1	0	1	0	1	1	0
7	0	1	1	0	1	1	0
8	1	1	1	1	0	1	0

	1	2	3	4	5	6	7	8
f	0	0	0	0	0	0	0	1
g	0	1	1	1	1	1	1	0

 2. Write Boolean expression for the following circuits:




OR = +    AND = x

$$F = [A + CD] + [A + D'] \times [B' + D]$$


3. Draw the logic diagram corresponding to the following Boolean expression:

$$(AB + A'B')(CD' + C'D)$$

 

## Part 2: Using Vivado

 4. Use Vivado to write VHDL gate-level description encoder circuit shown below



### Code:


```
Library ieee;
use ieee.std_logic_1164.all;

entity encoder is
  port(D3,D2,D1,D0:in bit; y,x,v:out bit);
end encoder;

architecture logic of encoder is
begin
  y<= D3 or((not(D2) and D1);
  x<= D3 or D2;
  v<= D3 or D2 or D1 or D0;

end logic;
```

### Schematic in Vivado:

 

5. Write behavioral (testbench) description of a four-input encoder circuit shown in #4, above.

**Code:**

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Testbench_encoder IS
END Testbench_encoder;

ARCHITECTURE behavior OF Testbench_encoder IS
  COMPONENT MidTerm
    PORT(
      D3 : IN std_logic;
      D2 : IN std_logic;
      D1 : IN std_logic;
      D0 : IN std_logic;
      y : OUT std_logic;
      x : OUT std_logic;
      v : OUT std_logic );
  END COMPONENT;

  signal D3 : std_logic := '0';
  signal D2 : std_logic := '0';
  signal D1 : std_logic := '0';
  signal D0 : std_logic := '0';
  signal y : std_logic;
  signal x : std_logic;
  signal v : std_logic;

  BEGIN
    uut: MidTerm
      PORT MAP ( D3 => D3, D2 => D2, D1 => D1, D0 => D0, y => y, x => x, v => v );
    process stim_proc: process begin
      wait for 100 ns;
      D3 <= '1'; D2 <= '0'; D1 <= '0'; D0 <= '1'; wait for 10 ns;
      D3 <= '1'; D2 <= '1'; D1 <= '1'; D0 <= '1'; wait for 10 ns;
      D3 <= '0'; D2 <= '1'; D1 <= '1'; D0 <= '0'; wait for 10 ns;
      D3 <= '1'; D2 <= '1'; D1 <= '0'; D0 <= '1'; wait for 10 ns;
      D3 <= '1'; D2 <= '0'; D1 <= '1'; D0 <= '1'; wait for 10 ns;
      D3 <= '0'; D2 <= '0'; D1 <= '0'; D0 <= '1'; wait for 10 ns;
      D3 <= '0'; D2 <= '0'; D1 <= '0'; D0 <= '0'; wait for 10 ns;
    end process;
  END;
```

Output in Vivado:

