

# Homework 5

Wednesday, November 11, 2020 1:53 PM

"I pledge my honor I have abided by the Stevens Honor system."

Alex Jasinski

\*P4.3. The initial voltage across the capacitor shown in Figure P4.3 is  $v_C(0^+) = -10$  V. Find an expression for the voltage across the capacitor as a function of time. Also, determine the time  $t_0$  at which the voltage crosses zero.

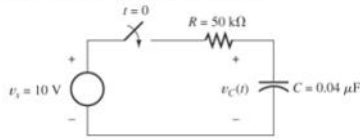


Figure P4.3

$$50,000 (.04 \times 10^{-6}) = .002$$

$$i_C = C \frac{dv_C}{dt}$$

$$-10 + 50,000 i_C + v_C = 0$$

$$50,000 C \frac{dv_C}{dt} + v_C = 10$$

$$\frac{dv_C}{dt} + \frac{v_C}{.002} = 5000$$

$$\frac{dv_C}{dt} + 500 v_C = 0$$

$$y_C = h e^{-50t}$$

$$y_C = h e^{-500t}$$

$$y_P = V_s$$

$$y_P = 10$$

$$y = y_C + y_P$$

$$v_C = h e^{-500t} + 10$$

$$\text{when } t=0, v = -10$$

$$-10 = h e^{-500(0)} + 10$$

$$h = -20$$

$$\text{When } v_C = 0:$$

$$0 = 10 - 20 e^{500t}$$

$$e^{500t} = \frac{1}{2}$$

$$t = .00139 \text{ s.}$$

P4.13. Derive an expression for  $v_C(t)$  in the circuit of Figure P4.13 and sketch  $v_C(t)$  to scale versus time.



Figure P4.13

$$i_C = C \frac{dv_C}{dt}$$

$$10 \times 10^{-3} = .01 \text{ A.} \quad RC = .02$$

$$RC \frac{dv_C}{dt} + v_C = .01$$

$$\frac{dv_C}{dt} + 50 v_C = \frac{1}{2}$$

$$\frac{dv_C}{dt} + 50 v_C = 0$$

$$v_C = h e^{-50t}$$

$$\text{When } t=0, h = v_C$$

$$v_C \rightarrow V_{\text{source}}$$

$$\text{where } i_C = 0$$

$$\text{so } h = v_C = \frac{1}{2} R$$

$$V_r = .01(2000)$$

$$v_C = 20 e^{-50t}$$

$$V_c = .01(2000)$$

$$V_c = 20$$

**P4.24.** The circuit shown in Figure P4.24 has been set up for a long time prior to  $t=0$  with the switch closed. Find the value of  $v_C$  prior to  $t=0$ . Find the steady-state value of  $v_C$  after the switch has been opened for a long time.


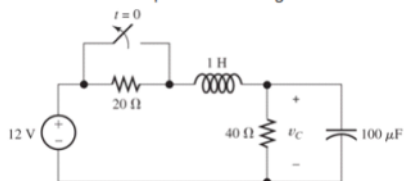


Figure P4.24

Before  $t=0$ :

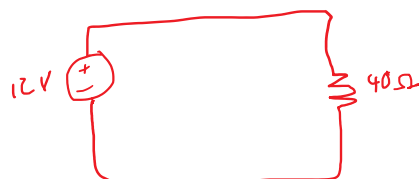

$$V_c = 12V$$

After  $t=0$ :



$$V_c = \frac{40}{60} 12$$

$$V_c = 8V$$

**P4.25.** Solve for the steady-state values of  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$ , and  $v_C$  for the circuit shown in Figure P4.25, assuming that the switch has been closed for a long time.

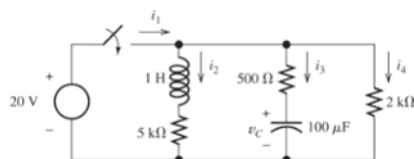


Figure P4.25

When  $v_c = 20V$  (Fully charged),  $i_c = 0A$ .

$$i_3 = i_c$$

$$i_3 = 0A.$$

Req for remaining resistors:

$$R_{eq} = \frac{10}{7} k\Omega$$

$$\left( \frac{5(2)}{5+2} \right)$$

For  $i_1$ :

For  $i_2$ :

For  $i_3$ :

For  $i_1$ :

$$V_s = i_1 R_{eq}$$

$$20 = i_1 \left( \frac{10}{7} \times 10^{-3} \right)$$

$$i_1 = .014 \text{ A.}$$

For  $i_2$ :

$$i_2 = \frac{2000}{7000} (.014)$$

$$i_2 = .004 \text{ A.}$$

For  $i_3$ :

$$i_3 = \frac{5000}{7000} (.014)$$

$$i_3 = .010 \text{ A.}$$

\*P4.34. Consider the circuit shown in Figure P4.34. The initial current in the inductor is  $i_L(0^-) = -0.2 \text{ A}$ . Find expressions for  $i_L(t)$  and  $v(t)$  for  $t \geq 0$  and sketch to scale versus time.


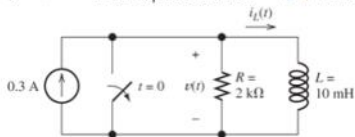


Figure P4.34

$$V_s = 2000 (.3)$$

$$V_s = 600 \text{ V.}$$

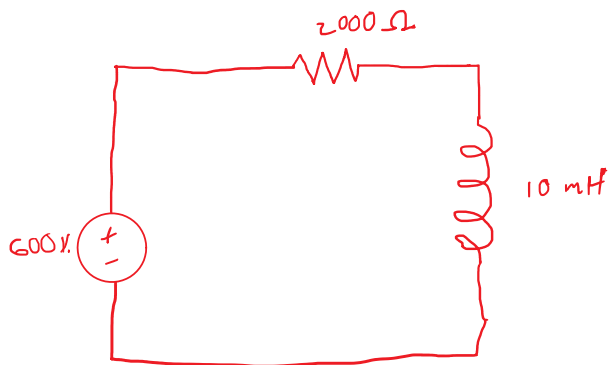

$$i(t) = .3 - .5 e^{-200000t}$$

$$V_L = L \frac{di_L}{dt} \quad 10 \times 10^{-3} = .01$$

$$-600 + 2000 i_L + .01 \frac{di_L}{dt} = 0$$

$$\frac{di_L}{dt} + 200000 i_L = 60000$$

$$y_c = K e^{-200000t}$$

$$y_p = i_s$$

$$y_p = .3$$

$$i(t) = .3 + K e^{-200000t}$$

$$\text{At } t=0, i(t) = -.2 \text{ A}$$

$$-.2 = .3 + K$$

$$K = -.5$$

$$V(t) = L \frac{di}{dt}$$

$$V(t) = 200000 (.5) e^{-200000t}$$

$$V(t) = 100000 e^{-200000t}$$

$$V(t) = 200000(0.5)e^{-}$$

$$V(t) = 100000e^{-200000t}$$

**P4.39.** The circuit shown in Figure P4.39 is operating in steady state with the switch closed prior to  $t=0$ . Find expressions for  $i_L(t)$  for  $t < 0$  and for  $t \geq 0$ . Sketch  $i_L(t)$  to scale versus time.

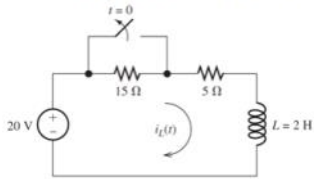


Figure P4.39

$$R_{eq} = 20\Omega$$

$$y_c = ke^{-10t}$$

$$-20 + 20i_L + 2\frac{di_L}{dt} = 0$$

$$y_p = i_s$$

$$i_s = 1A.$$

$$\frac{di_L}{dt} + 10i_L = 10$$

$$i(t) = ke^{-10t} + 1$$

Steady state current:

$$\frac{20}{5} = 4A.$$

$$4 = k + 1$$

$$k = 3$$

$$i(t) = 3e^{-10t} + 1$$

$$\text{for } t \geq 0$$

$$i(t) = 4 \text{ for } t < 0$$